



بسم الله الرحمن الرحيم

Project Title: Transistor-Level 4-BIT ALU Design

Module: 8-BIT REGISTER UNIT
Design

- Author: Ahmed Assem Mohamed

1. Abstraction

This report presents the design and implementation of an 8-bit register, a critical component in sequential digital systems. The register is used to store an 8-bit value synchronously with a clock signal and is implemented using eight cascaded D flip-flops at the transistor level using **MOSFET** technology, leveraging **130nm CMOS technology**. The circuit was meticulously developed and simulated using Cadence Virtuoso.

2. Logic Function and Truth Table


- Truth table(per bit)

CLK ↑	Di	Qi (after edge)
Rising	0	0
Rising	1	1
No edge	X	Qi (unchanged)

- Logical Behavior
At each CLK rising edge:
 $Q[7:0] \leq D[7:0]$.

3. Circuit Design


3.1. Schematic

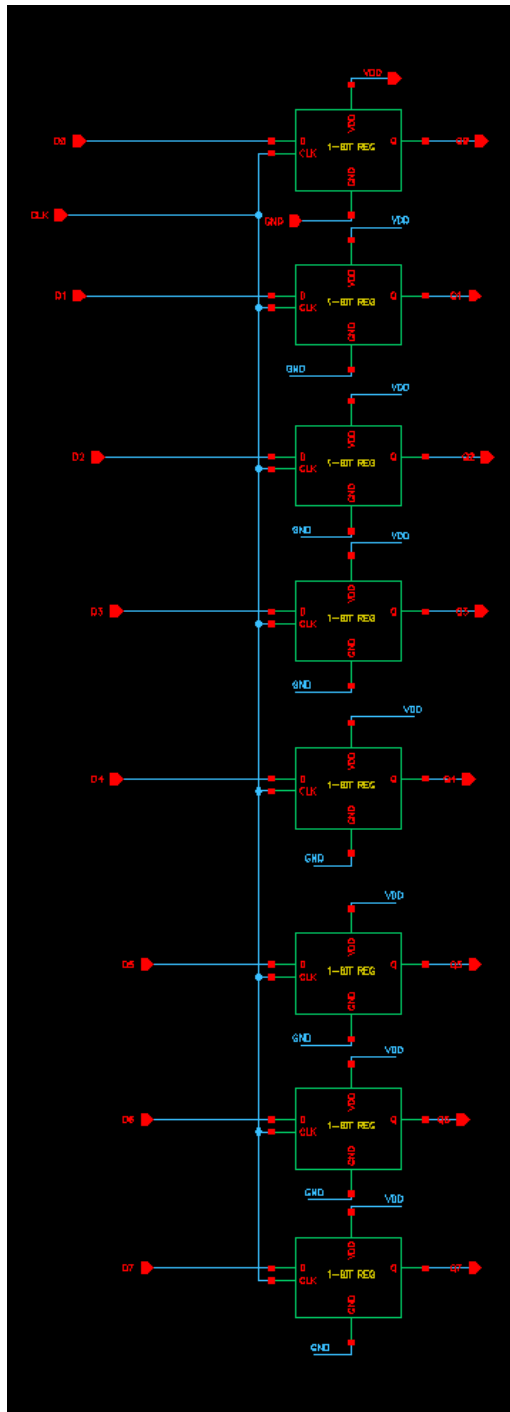

3.2. Design Approach

- 130nm CMOS process
- 1.2V VDD
- INPUTS: D0, D1, D2, D3, D4, D5, D6, D7, CLK
- OUTPUT: Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7
- Input Parameter: WN_REG
- Sizes: WN_REG

3.3. Symbol

 

4. Simulation and Results

- Timing parameters and waveforms will be the same as 1-bit register.