



بسم الله الرحمن الرحيم

Project Title: Transistor-Level 4-BIT ALU DESIGN

Module: 4-BIT ALU UNIT
Design

- Author: Ahmed Assem Mohamed

1. Abstraction

This report presents the design and implementation of a **4- Bit Arithmetic Logic Unit (ALU)** using 130nm **CMOS** technology. The ALU can perform both arithmetic and logical operations. Control logic allows the selection between these two classes of operations via the most significant bit (MSB) of a 4-bit selection line. The circuit was meticulously developed and simulated using Cadence Virtuoso.

2. Logic Function and Truth Table

Sel[3:0]	Mode	Operation	Output = $f(A, B)$	Notes
0000	Arithmetic	Increment A	$A + 1$	Wraps around on overflow
0001	Arithmetic	Increment B	$B + 1$	Wraps around on overflow
0010	Arithmetic	Transfer A	A	Pass-through
0011	Arithmetic	Transfer B	B	Pass-through
0100	Arithmetic	Decrement A	$A - 1$	Wraps around on underflow
0101	Arithmetic	Multiply A and B	$A \times B$	8-bit result shown
0110	Arithmetic	Add A and B	$A + B$	4-bit result
0111	Arithmetic	Subtract A - B	$A - B$	A assumed $\geq B$
1000	Logic	1's Complement A	$\sim A$	Bitwise NOT

1001	Logic	1's Complement B	$\sim B$	Bitwise NOT
1010	Logic	AND	$A \& B$	Bitwise AND
1011	Logic	OR	$(A B)$	Bitwise OR
1100	Logic	XOR	$A \wedge B$	Bitwise XOR
1101	Logic	XNOR	$\sim(A \wedge B)$	Bitwise XNOR
1110	Logic	NAND	$\sim(A \& B)$	Bitwise NAND
1111	Logic	NOR	$\sim(A B)$	Bitwise NOR


Some sample test cases. Example Input/Output Combinations
(for A = 0101 (5), B = 0011 (3))

Sel[3:0]	Operation	Output (Binary)	Output (Decimal)
0000	A + 1	0110	6
0001	B + 1	0100	4
0010	Transfer A	0101	5
0011	Transfer B	0011	3
0100	A - 1	0100	4
0101	A \times B	00001111 (15)	15
0110	A + B	1000	8
0111	A - B	0010	2
1000	$\sim A$	1010	10
1001	$\sim B$	1100	12
1010	A & B	0001	1
1011	A B	0111	7
1100	A \wedge B	0110	6
1101	$\sim(A \wedge B)$	1001	9

1110	$\sim(A \& B)$	1110	14
1111	$\sim(A B)$	1000	8

3. Circuit Design

3.1. Schematic

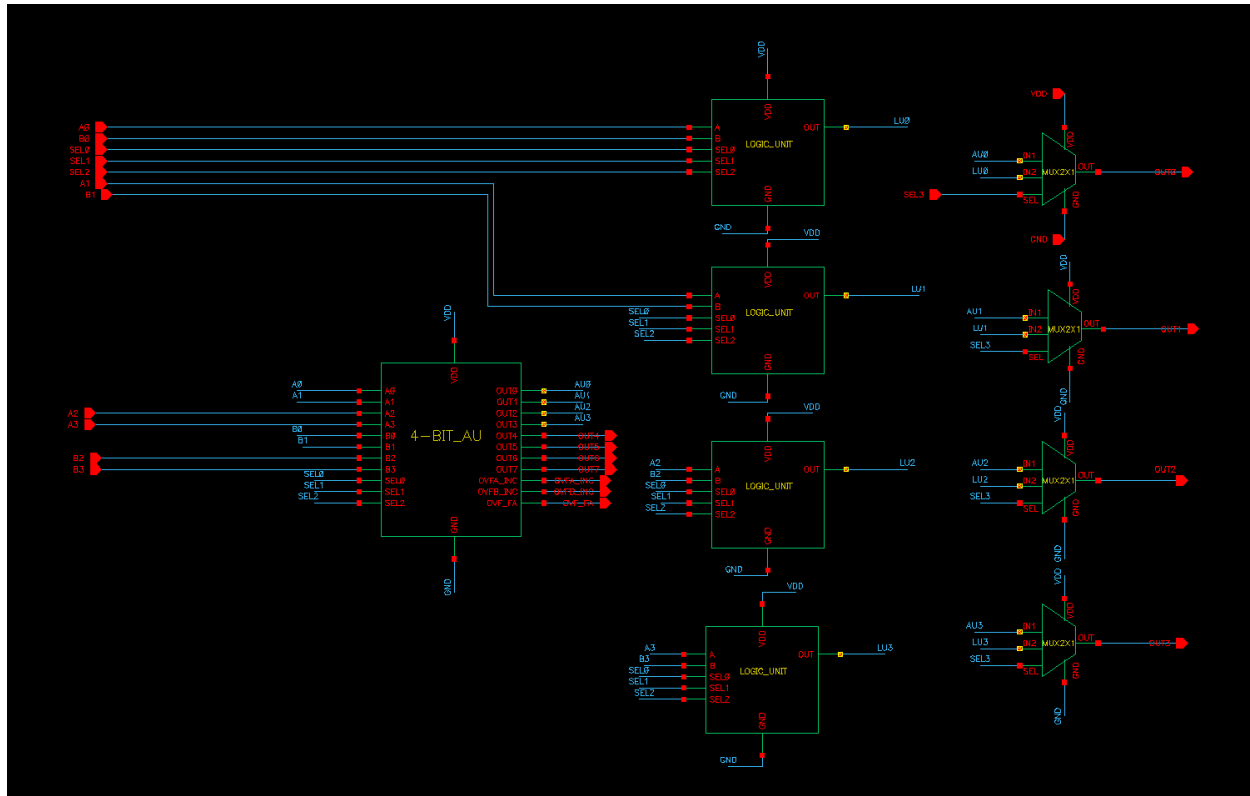


3.2. Design Approach

- 130nm CMOS process
- 1.2V VDD
- INPUTS: 4-BIT IN0, 4-BIT IN1, 4 SEL
- OUTPUTS: 8-BIT OUT, 3-BIT OVF
- Input parameter: WN_ALU
- Sizes: All gates have this size(even if it is the parameter for MUX-8X1) why? as already each gate is designed alone,

which is suitable size, this parameter is only to reduce number of variables

- Design Approach: 4-BIT ALU is the integration between 4*(1-BIT LU), 1*(4-BIT AU), and 4*(MUX_2X1)
- Although there is 8-bit output, all these bits are important only with MUL-circuit, for the rest of operations only the first 4 is important.
- OVF Flags: OVFA_INC, OVFB_INC, OVFA_INC
The first one is used only with FA-circuit, The second one is used only with INC/DEC-circuit for A input, The third one is used only with INC-circuit for B input.
- NOTE: OVF flags are designed on the assumption that the inputs are signed numbers.

3.3. Symbol

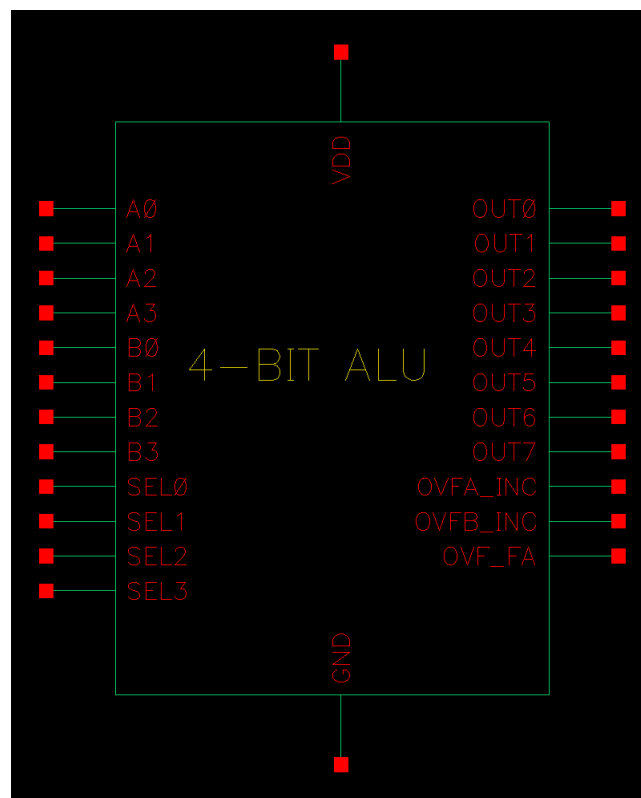


4. Simulation and Results

Inputs

Transient Analysis `tran`: time = (0 s -> 600 ns)


1

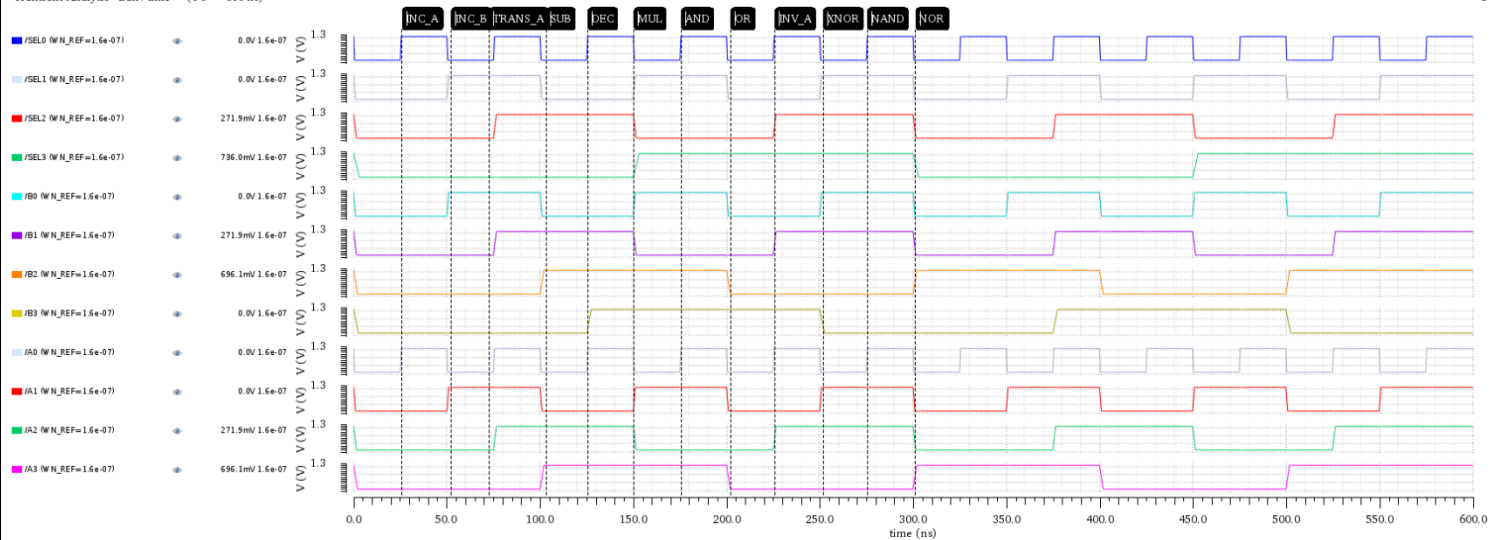

Outputs

Transient Response

Tue May 13 09:09:19 2025 1

 

Note: the simulation result is performed with a max input $f = 20.0\text{MHz}$