



بسم الله الرحمن الرحيم

Project Title: Transistor-Level OR Gate Design

- Author: Ahmed Assem Mohamed

1. Abstraction

This report presents the design and implementation of a OR gate at the transistor level, leveraging 130nm MOSFET technology. The circuit was meticulously developed and simulated using Cadence Virtuoso.


2. Logic Function and Truth Table

$$Y = (IN0 \mid IN1)$$

IN0	IN1	Y (IN0 OR IN1)
0	0	0
0	1	1
1	0	1
1	1	1

3. Circuit Design


3.1. Schematic

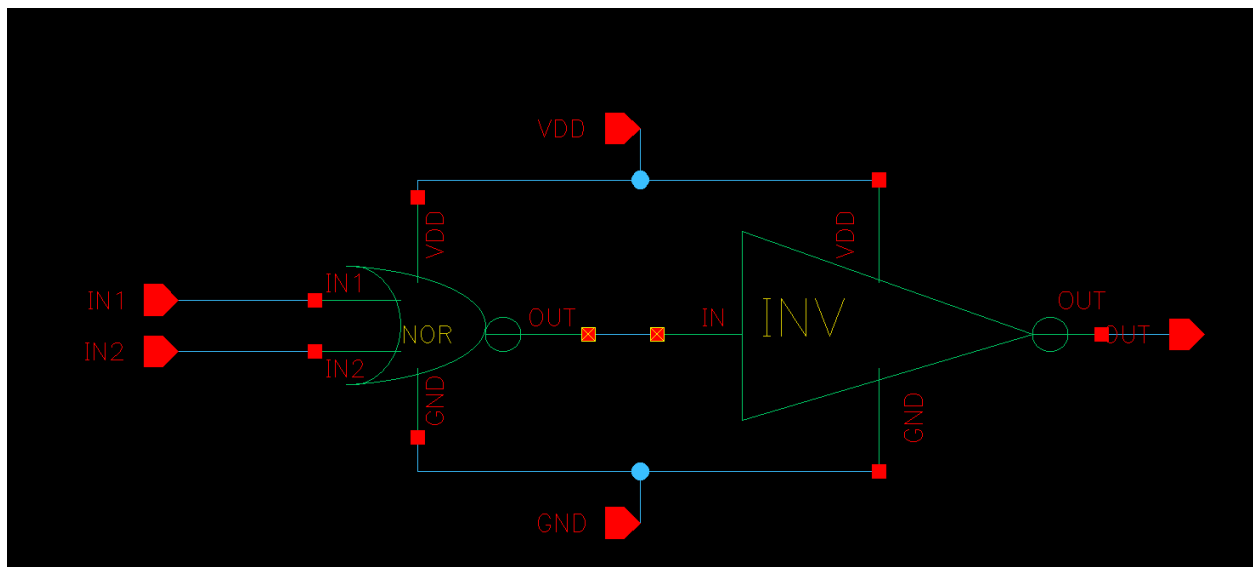


3.2. Design Approach

- 130nm CMOS process
- 1.2V VDD
- INPUTS: IN0, IN1
- OUTPUT: OUT
- Input Parameter: WN_OR
- Sizes: the same as NOR, but for the INV: NMOS has $1.6 \cdot \text{WN_OR}$, PMOS has $1.6 \cdot 1.8 \cdot \text{WN_OR}$
- why 1.6? NOR should be lower, to avoid wasting extra power in charging and discharging its own capacitance.
- while assuming $CL = 15 \cdot C_{REF}(\text{INV})$, $g \cdot f$ is approximately 4, so size of the OR = $0.6 \cdot \text{OR_ref}$, since $\text{WN_OR_ref} = \text{WN_INV}$ therefore $\text{WN_INV} = 1.6 \cdot \text{WN_OR}$.

3.3. Symbol

 

4. Simulation and Results

 

Note: the simulation result is performed with an input $f = 1.0\text{GHz}$ for IN1, while for IN2 $\frac{1}{3} * f$