



بسم الله الرحمن الرحيم

Project Title: Transistor-Level NOR Gate Design

- Author: Ahmed Assem Mohamed

1. Abstraction

This report presents the design and implementation of a NOR gate at the transistor level, leveraging 130nm MOSFET technology. The circuit was meticulously developed and simulated using Cadence Virtuoso.


2. Logic Function and Truth Table

$$Y = \sim(IN0 \mid IN1)$$

IN0	IN1	Y (IN0 NOR IN1)
0	0	1
0	1	0
1	0	0
1	1	0

3. Circuit Design


3.1. Schematic

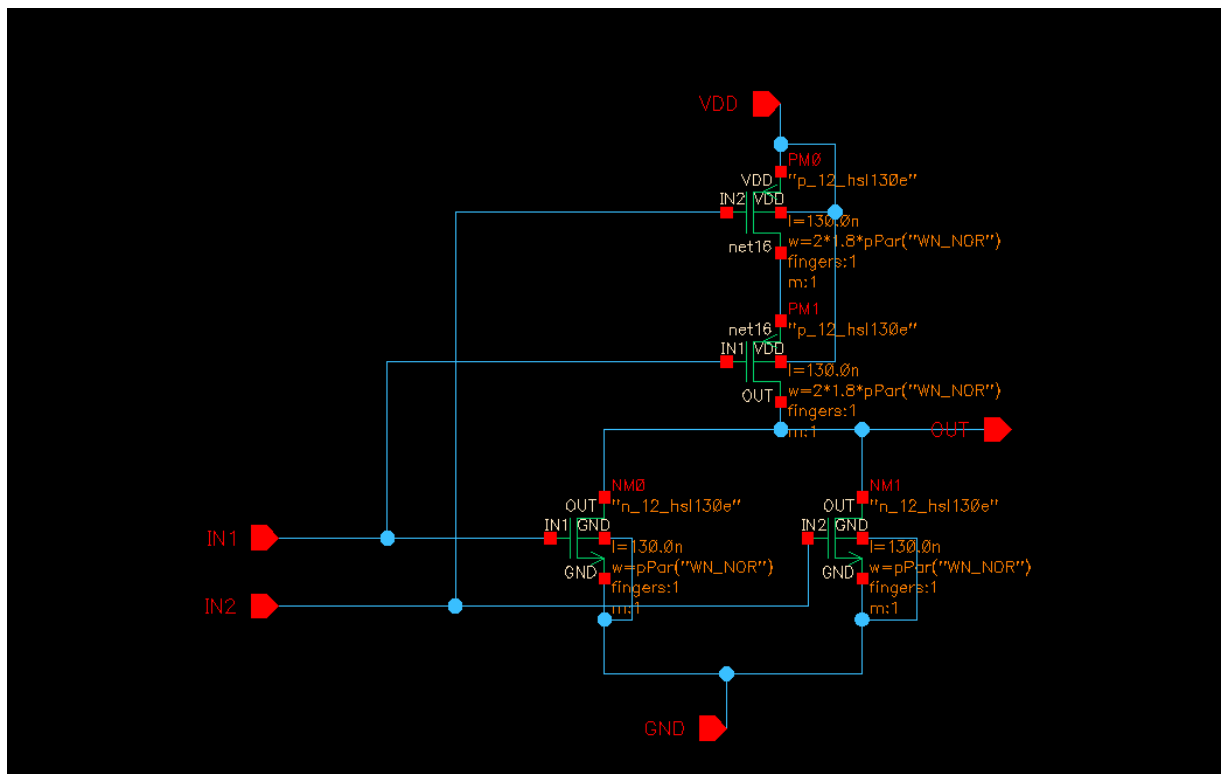


3.2. Design Approach

- 130nm CMOS process
- 1.2V VDD
- INPUTS: IN0, IN1
- OUTPUT: OUT
- Input Parameter: WN_NOR
- Sizes: the two NMOS have the dimensions WN_NOR, while the two PMOS have the dimensions $1.8 \times 2 \times \text{WN_NOR}$
- why 1.8? (came from simulation of the basic INV) therefore a symmetric INV. Note: now g(Logical effort) of NOR = 1.64
- why two? to have the same R-ON of the ref INV.

3.3. Symbol

 

4. Simulation and Results

 

Note: the simulation result is performed with an input $f = 333.3\text{MHz}$ for IN1, while for IN2 $\frac{1}{3} * f$